



Revisions		Title		Filename:	
Date	Name	Date	Name	PSU SW 807.gbr	Sheet of:
5-8-2005	Ju-3b	01-31-2005	Ju-3b		1 of 1
				Power supply for 100 Watt Sw Tube Transmitter	
				Number:	

The power supply

For this transmitter I use a Simple Power supply with less components. I use two separate transformers, one for the oscillator and buffer tube, and one for the final tubes.

The transformer I use for the high voltage has secondary only 250 volt. I use a doubler to get the 700 volt. if You have one with 280 volt this would be better. This will give you at the end the 750 volt you need for the 100 watt power.

Of course You can use a choke and extra capacitor in both circuits, but when U use the 220uF capacitors this is not neccercery.

Components

C1 = 220 μ (400Volt)
C2 = 220 μ (400Volt)
C3 = 220 μ (450Volt)

D1 = 1N4007 ((1000V/1A))
D2 = 1N4007 ((1000V/1A))
D3 = 1N4007 ((1000V/1A))
D4 = 1N4007 ((1000V/1A))
D5 = 1N4007 ((1000V/1A))
D6 = 1N4007 ((1000V/1A))

F1 = 1000mA
F2 = 2A
F3 = 500mA

S1-S2 = Switch
S3-S4 = Switch

Tr1 = 250V/300mA
Tr2 = 2*280V/120mA